Assignment-2

Anjrudha Rukavni 2019CS SO421

· Overview of Design:-

· A clock that can display HH: MM: 85 at given instance:

· Format of displays:- H, Ho: Ma Mo: S, So.


2. MM SS.

- Evnen resetted starts from 00:00:00 and counts till 23:89:89 and then again starts from 00:00:00.
 - Push buttons:-
 - 1. KI. Changer to display format of display, remains in the state even after released
 - Displaying mmiss only till button was pressed was also a good idea but not user friendly,
 - d. K2. Enters into edit mode.
 Default courses is at H;
 - 3. kg Changer cursor for right.

 H, -> Ho-> M, -> Mo +> S, -> So
 - 4. K4- Inovements corrent number ai-
 - 5. K5- reset everything to 0.

- · Displaying of numbers as per mode.
 - At any point all 81x values are stored.
 - when calted by
 - 4 of them are displayed on 7-segment display.
 - When HH: MM mode is ap, a dot is also shown which is blinking at 1 Hz to indicate clock is working and is in HH: MM mode.
- state diagram: (triggered by rising edge of kg),
 for rotating wirson location as key is pressed
 States: H1, H0, M1, M0, S1, S0.
 trigger: kz

Output: - Cursor location.

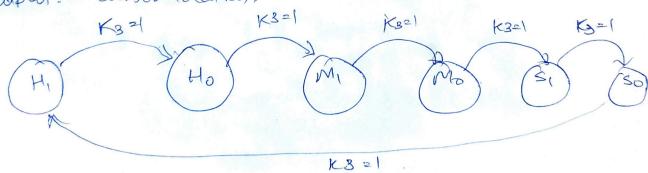

· As its triggered by edge of 123, multiple changes will not occur for strigle per button press.

· Multiple buton prestings:-

- Only first pressing is considered.

- All others pressed are ignored till initially pressed is released.

· Edit mode display:-

- Current position of cursor is denoted by blinking the number at 1Hz. making it easier to identify

- when cursor is shafted to see: Si, display mode is changed to mm: S& format.

· BCD to 7- segment display. is_dot is dot Bep ABCOEFGH 1 0000 0 1 , 00000010 0001 0 90011110 Q r 0010 00 100 100 3, 00001100 0 0011 Ce, 10011000 0 100 6 100 1000 0 0101 0110 01000000 7. 0111 000/11/0 0 000000000 1000 9. 00001000 0 1001 (0, H bit is changed to 1. When isolat= a Similarly

friquency for dot is maintained at 1 Hz and Duration between refresher (Refresh period) is maintained at 10-5 mg.

clarko mitz reset Ky K3 K2 K1 clock 15 Button reset 1 1 K4 61 Ledit mode Display mode counter reset 1 the Mr. Tho FSM Display roode LUNGA Clock 10 Hz Display driver Selector-gen selected out Solution BCD_to_7 Segment B (including dot) andode o cathodes